

## EE 110, Winter 2016, Design Project: due March 09, 2016 in class

**Goal:** Your fancy audio system is powered by a so-called “switching mode power supply (SMPS)” that corrupts (adds) an undesired 10kHz signal to the audio signal (10Hz–50kHz) that you desire to amplify and eventually send to your speakers. Your goal is to design a circuit that removes the 10kHz signal from the corrupted signal.

**Recommended Circuit:** You will need a so-called notch or band-reject filter with a center frequency of ~~60Hz~~ 10kHz. Figure 1 shows an example circuit that you may want to consider.

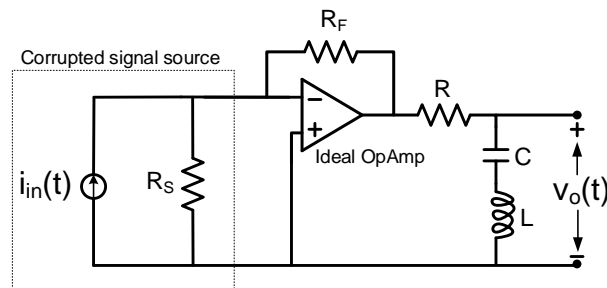


Figure 1

### Specifications:

1. The corrupted signal is available as a current source with source impedance of 10 kOhms
2. The output of your circuit should be a voltage signal
3. Notch bandwidth should be  $\leq 2\text{kHz}$
4. For  $10\mu\text{A}$  amplitude sinusoidal input in the passband, output sinusoidal voltage amplitude should be 100mV
5. For  $10\mu\text{A}$  10kHz sinusoidal input, the output sinusoidal amplitude should be  $\leq 2\text{mV}$

### Constraints:

1. The only inductors available to you are  $L=100\text{mH}$  inductors with a series resistance of 10 Ohms (not shown in Figure 1)
2. Do not use resistors larger than 200kOhms; using multiple 200kOhm resistors in series to realize a larger resistor is also not allowed.

### Assumptions:

1. Ideal operational amplifiers (infinite gain, infinite input impedance i.e. zero input current, zero output impedance) are available for your use.

### Suggested Procedure:

1. Derive the transfer function of your circuit to confirm that it is indeed a notch filter
2. Derive expressions for the notch frequency and the notch bandwidth (similar to the BPF case, as explained in class)
3. Derive an expression for the pass-band gain (far away from the desired notch frequency): this will tell you how large the sinusoidal output voltage amplitude would be for a given passband sinusoidal current input amplitude
4. Derive an expression for the stop-band gain (i.e. at the notch frequency): this will tell

you how large the sinusoidal output voltage amplitude would be for a given sinusoidal current input amplitude at the notch frequency

5. Using the expressions derived above and the given specifications and constraints, choose component values

#### **Deliverable Report:**

1. Expressions for your design formulae (transfer function, notch frequency, notch bandwidth, pass-band gain, and stop-band gain). A schematic of your design clearly showing the component values
2. Clearly marked Bode plots of the magnitude and phase response of the filter circuit you have designed.
3. Expected steady state output voltage for  $i_{in}(t) = 10\cos(2\pi \cdot 9 \times 10^3 t)$  uA.
4. An Appendix showing all derivations and calculations.

#### **Extra Credit (25% extra):**

1. Design to meet a revised, more stringent specification #5: the output sinusoidal voltage amplitude for 10μA 10kHz sinusoidal input should be  $\leq 20\mu V$

#### **Notes:**

1. The main report (excluding the amplitude) should be no more than 2 pages (single-sided).
2. The Appendix should be no more than 4 pages (single-sided). You will be graded based on your main report; the Appendix will be used mainly to prevent plagiarism.
3. You are not restricted to the recommended circuit shown in Figure 1. You are free to develop your own circuits. Transformers and dependent sources other than explicit OpAmps are not allowed.

#### **Change Log:**

Date	Changes
02/19/2016	Created original.
<u>02/22/2016</u>	<u>Fixed a typo in the “Recommended Circuit” section</u>
<u>02/22/2016</u>	<u>Fixed a typo in the “Specifications” section</u>
<u>02/24/2016</u>	<u>Fixed the same (as above) in the “Extra Credit” section</u>